

8-bit SAR ADC on Tiny Tapeout

tt06-sar

Goal

Walk you through **tt06-sar**, and the steps necessary to **tapeout** on **TinyTapeout**

Idea

Trigger (2009)

CONTRIBUTED
P A P E R

Analog Circuit Design in Nanoscale CMOS Technologies

Classic analog designs are being replaced by digital methods, using nanoscale digital devices, for calibrating circuits, overcoming device mismatches, and reducing bias and temperature dependence.

By LANNY L. LEWYN, Life Senior Member IEEE, TROND YTTERDAL, Senior Member IEEE, CARSTEN WULFF, Member IEEE, AND KENNETH MARTIN, Fellow IEEE



 


Fig. 6. A portion of an amplifier cell with regular device pitch in both X and Y directions (upper metal layers removed for clarity). For best HF performance, all devices' substrate ties are placed on either side of two-finger gate patterns. Grounded stripes of poly are interposed between device active area and all substrate ties to minimize the need for reticle compensation (OPC) and also reduce poly etch loading to achieve good CD accuracy.


Problem (2014)

 



Circuit

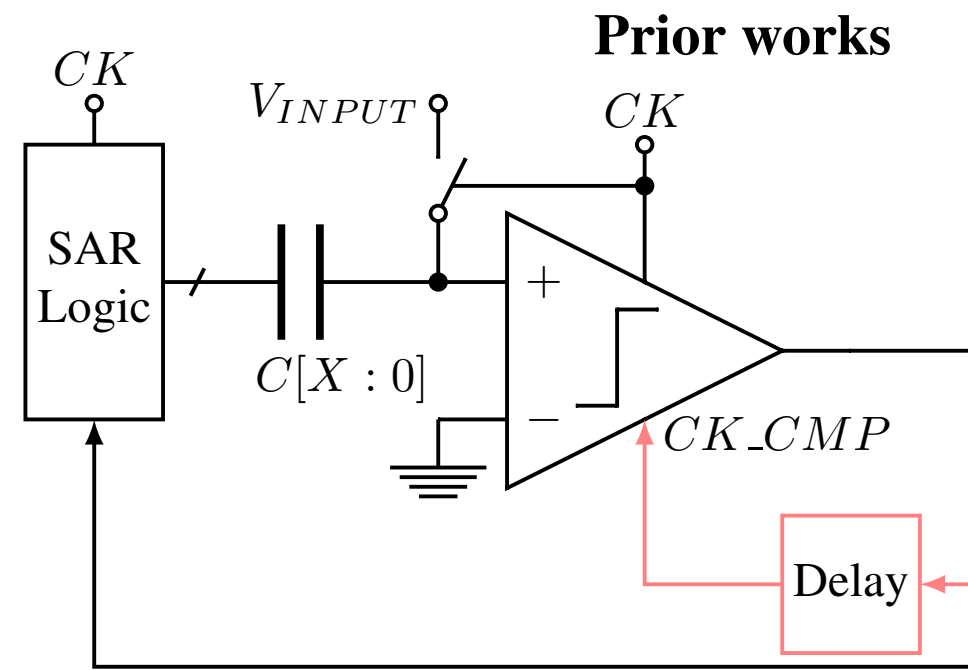



(a) Clock generation separate from CDAC

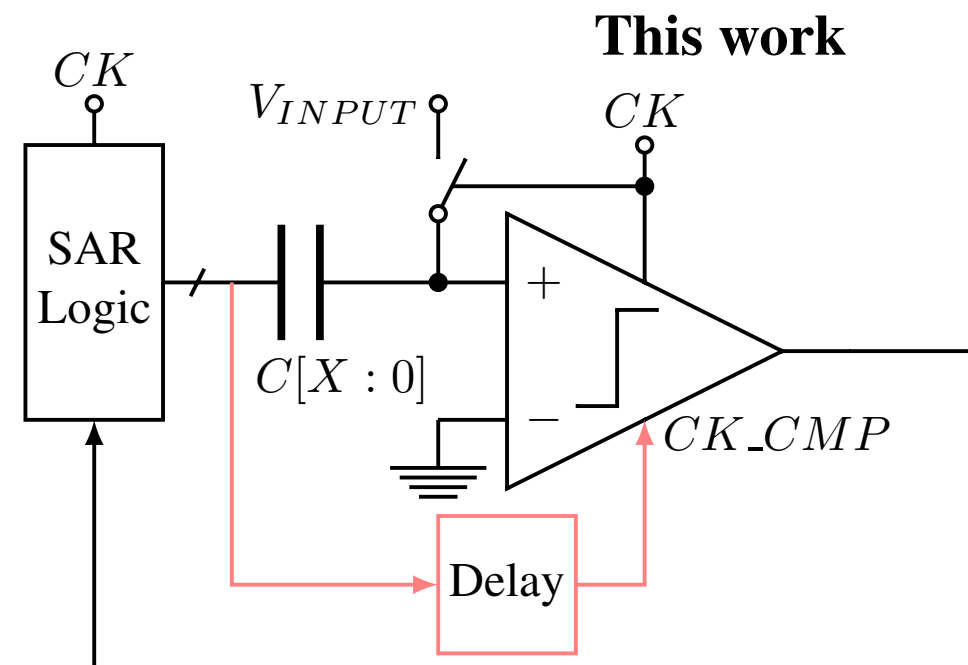

(b) Clock generation including CDAC

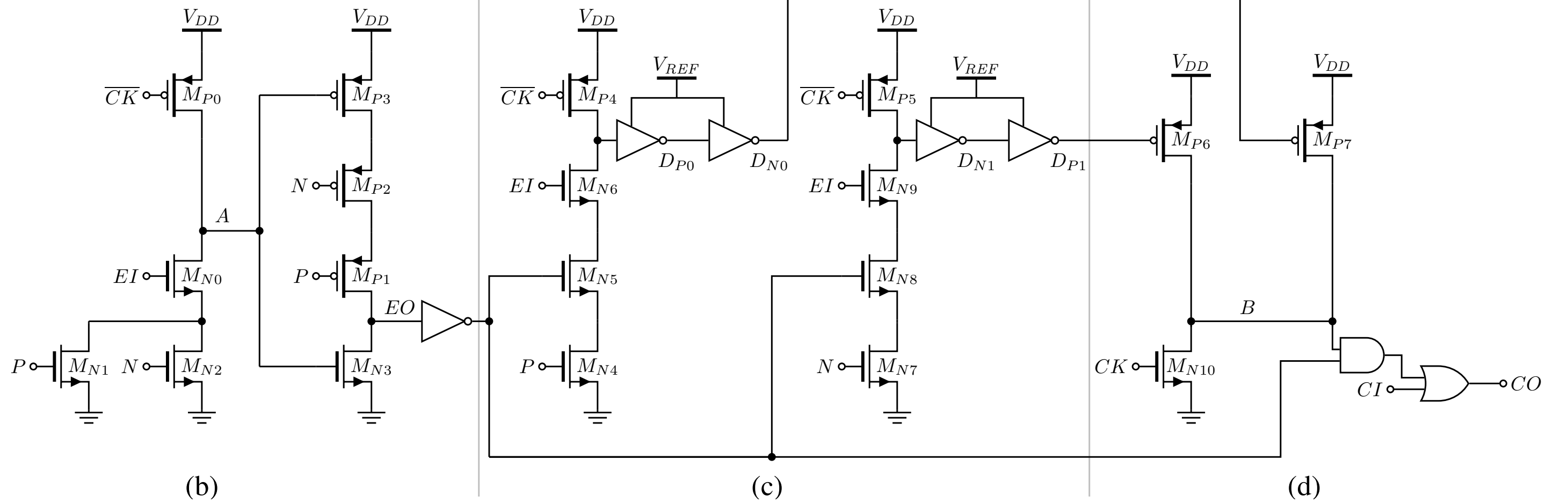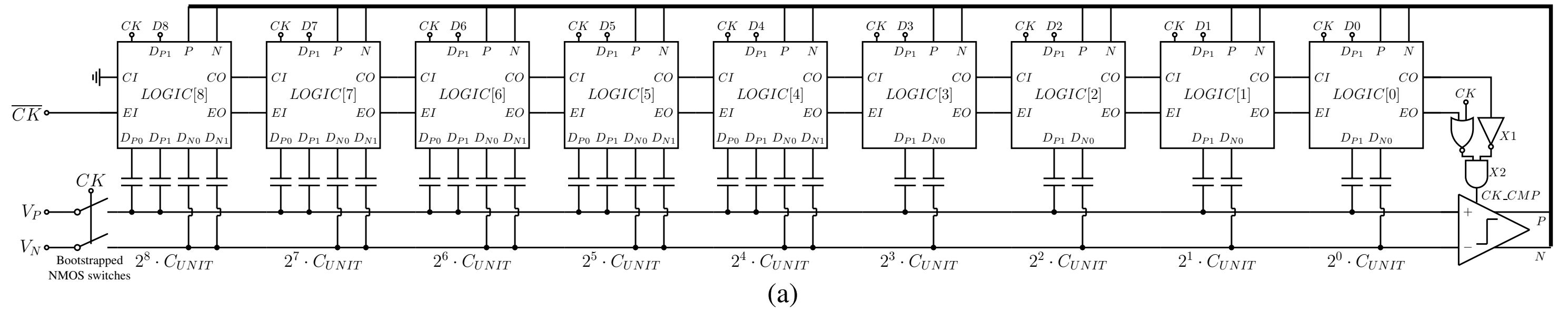


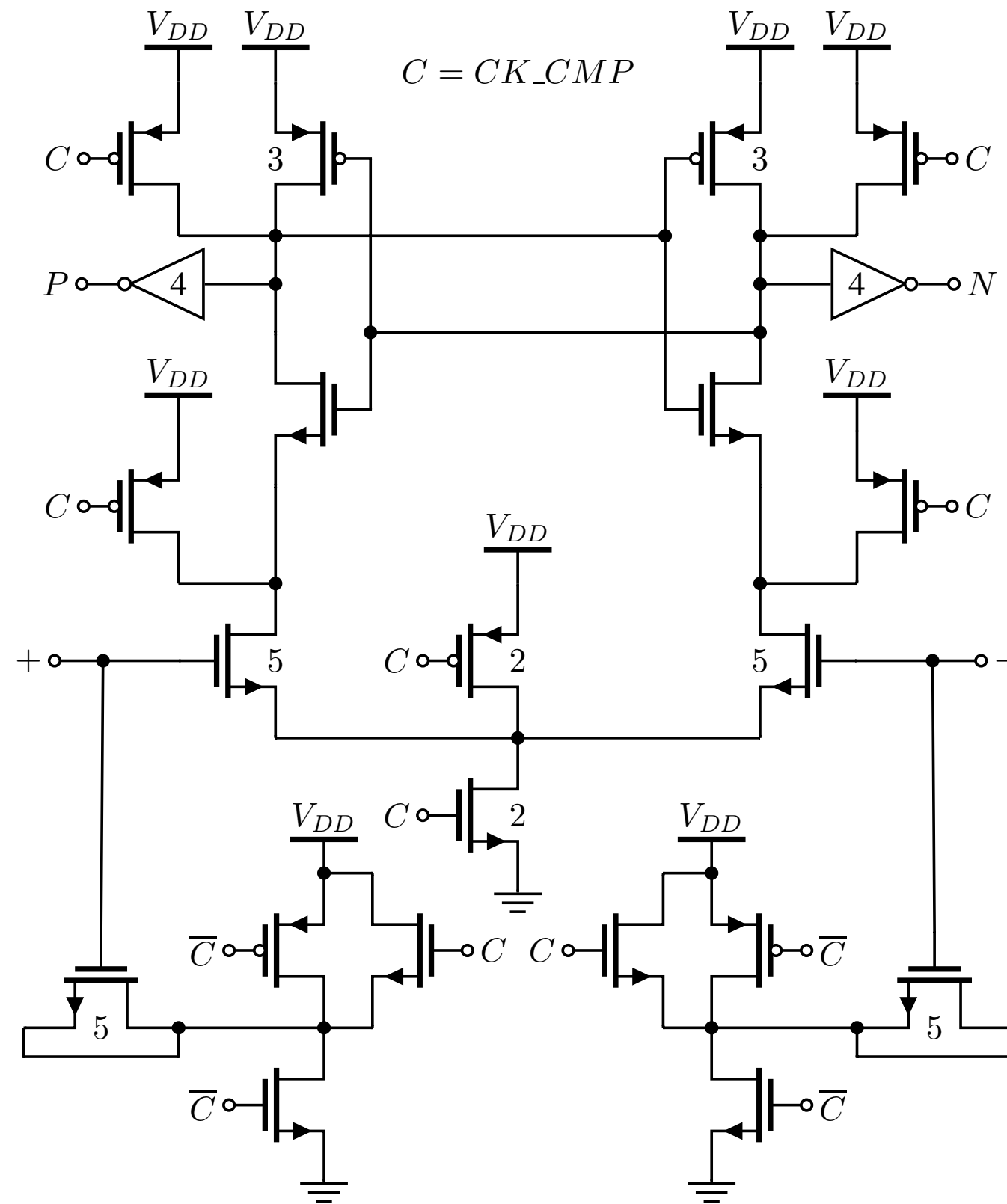

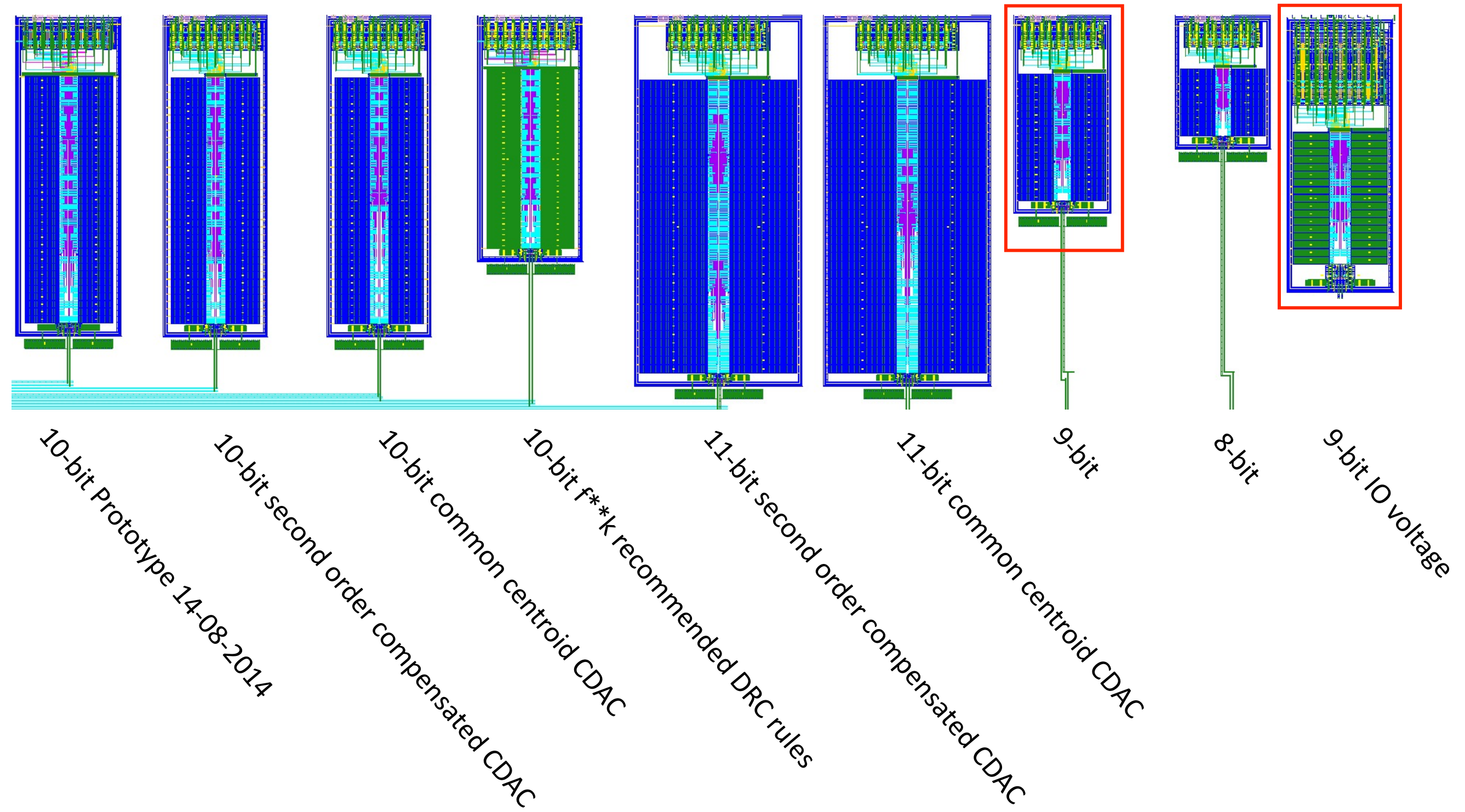

	Weaver [5]	Harpe [9]	Patil [10]	Liu [11]	This work	
Technology (nm)	90	90	28 FDSOI	28	28 FDSOI	
Fsample (MS/s)	21	2	No sampling	100	2	20
Core area (mm ²)	0.18	0.047	0.0032	0.0047	0.00312	
SNDR (dB)	34.61	57.79	40	64.43	46.43	48.84
SFDR (dBc)	40.81	72.33	30	75.42	61.72	63.11
ENOB (bits)	5.45	6.7 - 9.4	6.35	10.41	7.42	7.82
Supply (V)	0.7	0.7	0.65	0.9	0.47	0.69
Pwr (μ W)	1110	1.64 -3.56	24	350	0.94	15.87
Compiled	Yes	No	No	No	Yes	
FoM (fJ/c.step)	838	2.8 - 6.6	3.7	2.6	2.7	3.5

Compilation

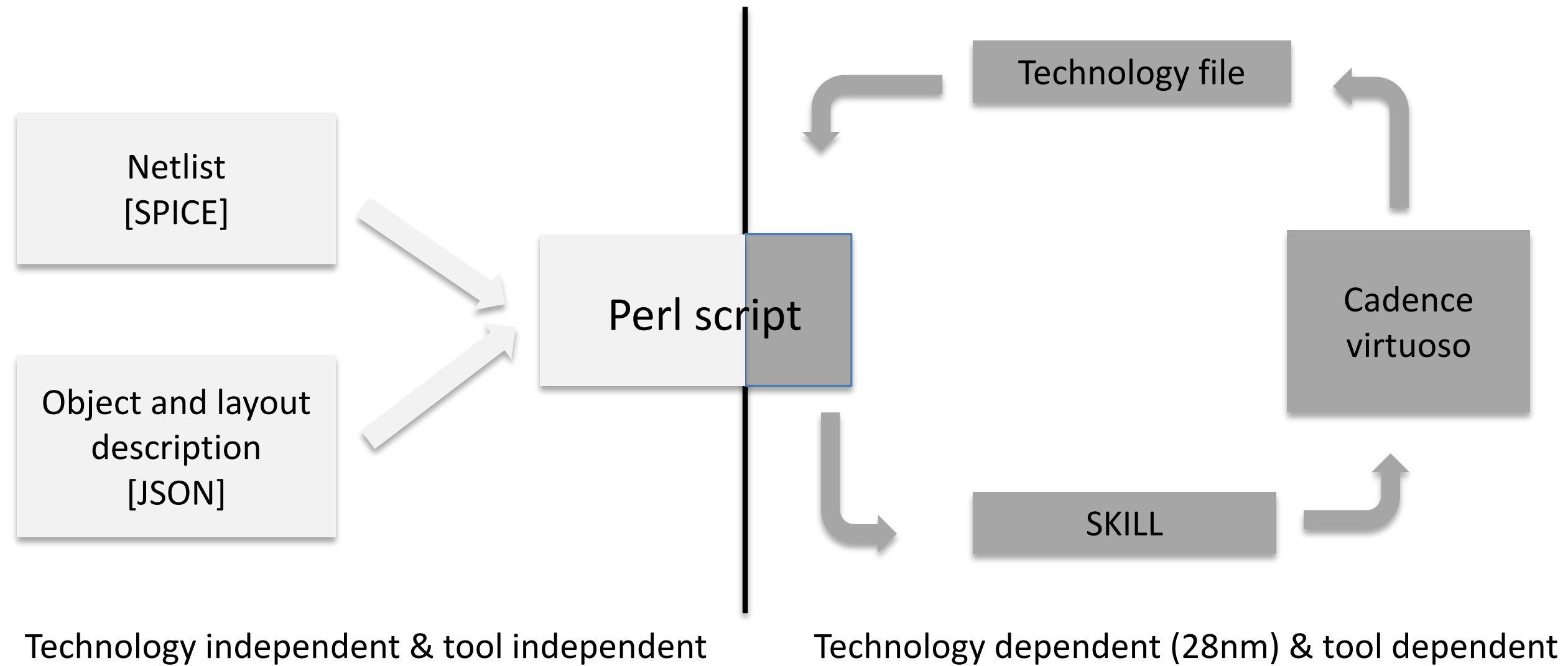


16 k Perl lines. Ported to C++ for speed ⇒ [ciccreator](#)


```

{ "name" : "DMOS" ,
  "class" : "Gds::GdsPatternTransistor",
  "yoffset": -0.5,
  "widthoffset" : -1,
  "fillCoordinatesFromStrings" : [
    [ "OD",
      "-----xxxx",
      "----xCxC-----xCxC",
      "----xxxx-----xxxx",
      "----xCxC-----xCxC",
      "-----xxxx"
    ],
    [ "PO",
      "-mmmmmmmmmmmmmmmm-----",
      "-----",
      "-mmmmmmmmmmmmCxC-----",
      "-----",
      "-mmmmmmmmmmmmmmmm-----"
    ],
    [ "M1",
      "-----xxxx",
      "----wDww-----xxxx",
      "-----wGww---xBxx",
      "----wSww-----xxxx",
      "-----xxxx"
    ]
  ]
}

```

- Structure and any other property is described in JSON (JavaScript Object Notation)
- “name” is the name of the cell
- “class” defines which object to use
- All other classes in the JSON object refer to object methods (there are some special functions, but more on that later)
- Convert a text string into a layout drawing
 - c = contact
 - C = center contact on rectangle left edge
 - x = fill rectangle
 - m = use minimum length poly
 - w = use “width” from techfile
 - DGSB = add ports

 

 

OD
 CO
 PO
 $M1$


```

{ "name": "IVX1_CV" ,
  "symbol" : "inv",
  "class" : "Layout::LayoutDigitalCell",
  "spice" : [
    ".subckt IVX1_CV A Y AVDD AVSS" ,
    "MN0 Y A AVSS AVSS NCHDL",
    "MP0 Y A AVDD AVSS PCHDL",
    ".ends IVX1_CV"],
  "addSchematicCoordinates" : {
    "MN0" : [ 0.25, 0, "R0"],
    "MP0" : [0.25, 0.5, "R0"]
  },
  "beforeRoute" : {
    "addDirectedRoutes" : [ ["M1","Y","MN:D-|--MP:D"], ["PO","A","MN:G-MP:G"] ]
  },
  "afterRoute" : {
    "addPortOnRects" : [ ["A","M1", "MN0:G"] , ["Y", "M1", "MN0:D"] ]
  }
}

```

What symbol to use, defaults to templates/skill/<name>.il


LayoutDigitalCell has extra functions for digital cells, and will add power rails.


Connectivity defined by SPICE. SPICE subcircuit can be read from a separate file

Help the schematic generator to place transistors so it's easier to read schematics

Find rectangle on device MN:D, and route in M1 to rectangle MP:D using a left, up or down, left pattern.

Add port for A on the gate of MN0

 

 


(a)

```
.SUBCKT SAREMX1_CV P N EI EO CK_N AVDD AVSS
MN0 N3 EI A AVSS NCHDL
MN1 N3 P AVSS AVSS NCHDL
MN2 AVSS N N3 AVSS NCHDL
MN3 EO A AVSS AVSS NCHDL
MP0 AVDD CK_N A AVSS PCHDL
MP1 N2 P EO AVSS PCHDL
MP2 N1 N N2 AVSS PCHDL
MP3 AVDD A N1 AVSS PCHDL
.ENDS
```

(b)

```
{ "name": "SAREMX1_CV",
  "class": "Layout::LayoutDigitalCell",
  "addConnectivityRoutes": [
    ["M1", "N1|N2", "||", ""], 1
    ["M1", "N3", "-|", ""], 2
    ["M1", "EO", "--|-", "onTopR"] 3
  ],
  "addDirectedRoutes": [
    ["PO", "P", "MN1:G-MP1:G"], 4
    ["PO", "N", "MN2:G-MP2:G"], 5
    ["PO", "A", "MN3:G-MP3:G"], 6
    ["M1", "A", "MN0:S-MP0:S"], 7
    ["M1", "A", "MP0:S-|--MP3:G"] 8
  ]
}
```

(c)

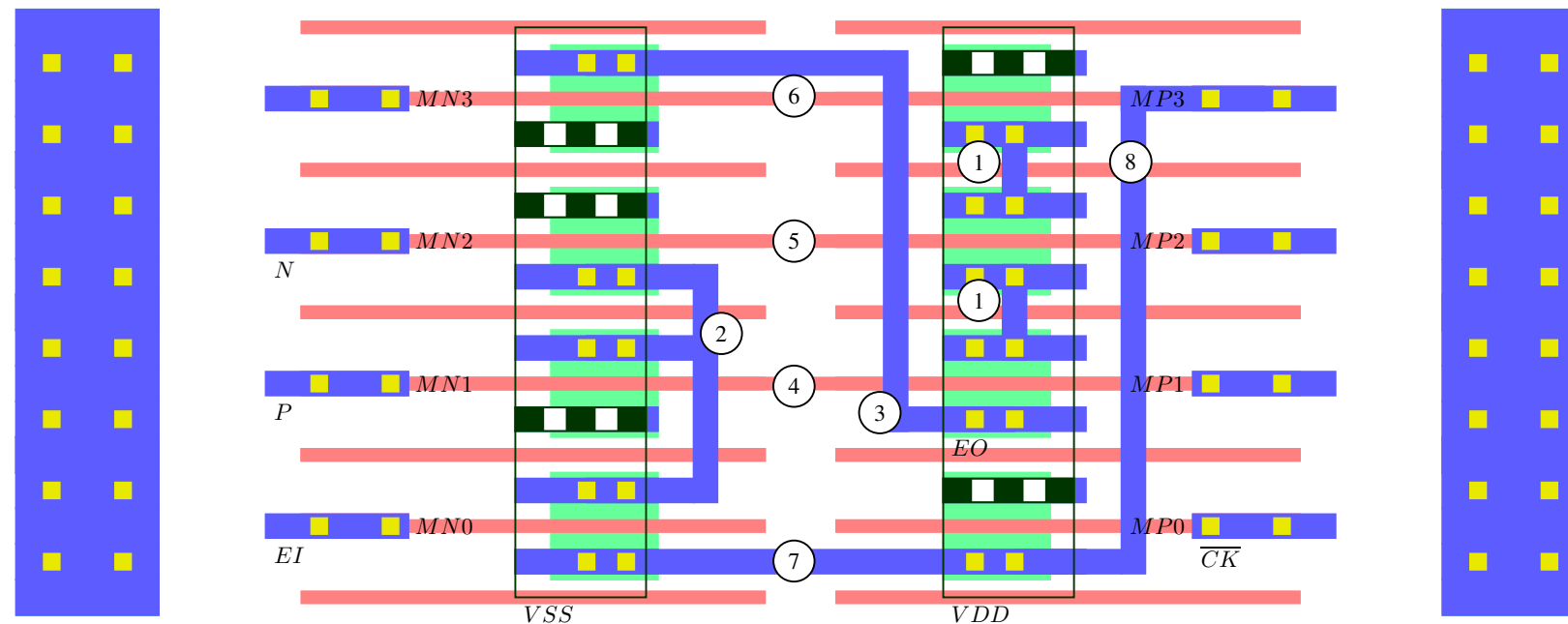


(d)

Since then

Measured: 28 nm FDSOI, 55 nm
Ported: 22 nm FDSOI, 22 nm, 28 nm, 65
nm, 130 nm

2022: There is an open source port to
skywater 130nm!

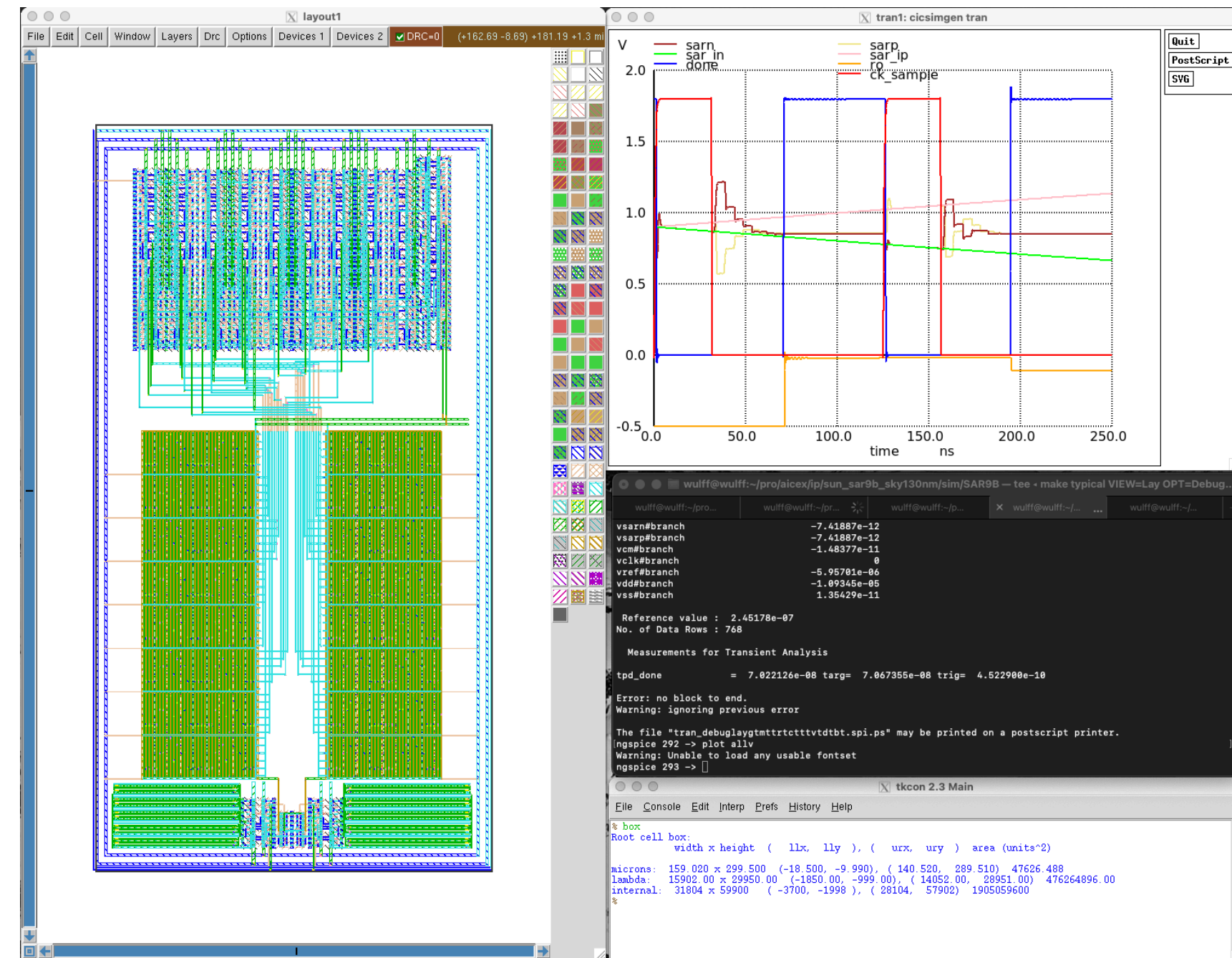[wulffern/sun_sar9b_sky130nm](https://github.com/wulffern/sun_sar9b_sky130nm)



Super simple transistor was a good
choice for portability

```
//sky130
{ "name" : "DMOS_BULK_N",
  "class" : "Gds::GdsPatternTransistor",
  "abstract" : 1,
  "yoffset" : -0.5,
  "widthoffset" : -0.5,
  "fillCoordinatesFromStrings" : [
    [ "OD",
      "-----",
      "----xxx-----",
      "----xxx-----",
      "----xxx-----",
      "-----"
    ],
    ...
    [ "M1",
      "-----xxx",
      "----wDw-----xxx",
      "-----wGw---xBx",
      "----wSw-----xxx",
      "-----xxx"
    ],
    ...
    [ "NDIFFC",
      "-----",
      "----LTR-----",
      "-----",
      "----LTR-----",
      "-----"
    ]
  ]
}
```

```
//28nm FDSOI
{ "name" : "DMOS",
  "class" : "Gds::GdsPatternTransistor",
  "yoffset" : -0.5,
  "type" : "pch",
  "widthoffset" : -1,
  "fillCoordinatesFromStrings" : [
    [ "OD",
      "-----xxxx",
      "----xxK-----xCxC",
      "----xxx-----xxxx",
      "----xxK-----xCxC",
      "-----xxxx"
    ],
    [ "PO",
      "-----",
      "-----",
      "-----mxc-----",
      "-----",
      "-----"
    ],
    [ "M1",
      "-----xxx",
      "----wDww-----xxx",
      "-----wGww---xBxx",
      "----wSw-----xxx",
      "-----xxx"
    ]
  ],
  "afterNew" : {
    "copyColumns" : [
      { "count" : 0, "offset" : 4, "length" : 4 }
    ]
  }
}
```


2016 (Perl compiler)

```
{ "name": "SARCMPHX1_CV",
  "description" : "Half a strong-arm comparator",
  "class" : "Layout::LayoutDigitalCell",
  "setYoffsetHalf" : "" ,
  "rows" : 7,
  "beforeRoute" : {
    "addDirectedRoutes" : [ ["P0", "VMR", "MN6:G-MP6:G"],
                           ["M1", "VMR", "MP4:G|MP6:G"],
                           ["M1", "CI", "MN1:G|MN5:G"],
                           ["M1", "N2", "MN1:D,MN3:D,MN5:D-|--MP1:D"],
                           ["M1", "N1", "MN0:D,MN2:D|-MN4:D"],
                           ["M1", "N1", "MN0:D-|--MP0:S"],
                           ["M1", "CO", "MP3:D,MP5:D--|-MN6:D"],
                           ["P0", "CK", "MN0:G-MP0:G"],
                           ["M1", "CK", "MP0:G,MP1:G-|MP3:G"],
                           ["M4", "NC", "MP2$:D-|--MP2:G"]
                         ],
  },
  "afterRoute" : {
    "addPortOnRects" : [ ["AVDD", "M4" ],
                        ["N1", "M1", "MN4:D"],
                        ["N2", "M1", "MN5:D" ] ]
  }
}
```

2022 (C++ compiler)

```
{ "name": "SARCMPHX1_CV",
  "description" : "Half a strong-arm comparator",
  "class" : "Layout::LayoutDigitalCell",
  "setYoffsetHalf" : 1 ,
  "rows" : 7,
  "meta" : {
    "noSchematic" : true
  },
  "decorator" : [
    {"ConnectSourceDrain" : ["M1", "||", ""]}
  ],
  "beforeRoute" : {
    "addDirectedRoutes" : [ ["P0", "VMR", "MN6:G-MP6:G"],
                           ["M1", "VMR", "MP4:G|MP6:G"],
                           ["M1", "CI", "MN1:G|MN5:G"],
                           ["M1", "N2", "MN1:D,MN3:D,MN5:D-|--MP1:D"],
                           ["M1", "N1", "MN0:D,MN2:D|-MN4:D"],
                           ["M1", "N1", "MN0:D-|--MP0:S"],
                           ["M1", "CO", "MP3:D,MP5:D--|-MN6:D"],
                           ["P0", "CK", "MN0:G-MP0:G"],
                           ["M1", "CK", "MP0:G,MP1:G-|MP3:G"],
                           ["M4", "NC", "MP2$:D-|--MP2:G"]
                         ],
  },
  "afterRoute" : {
    "addPortOnRects" : [ ["BULKP", "M1"],
                        ["BULKN", "M1"],
                        ["AVDD", "M4" ],
                        ["N1", "M1", "MN4:D"],
                        ["N2", "M1", "MN5:D" ] ]
  }
}
```

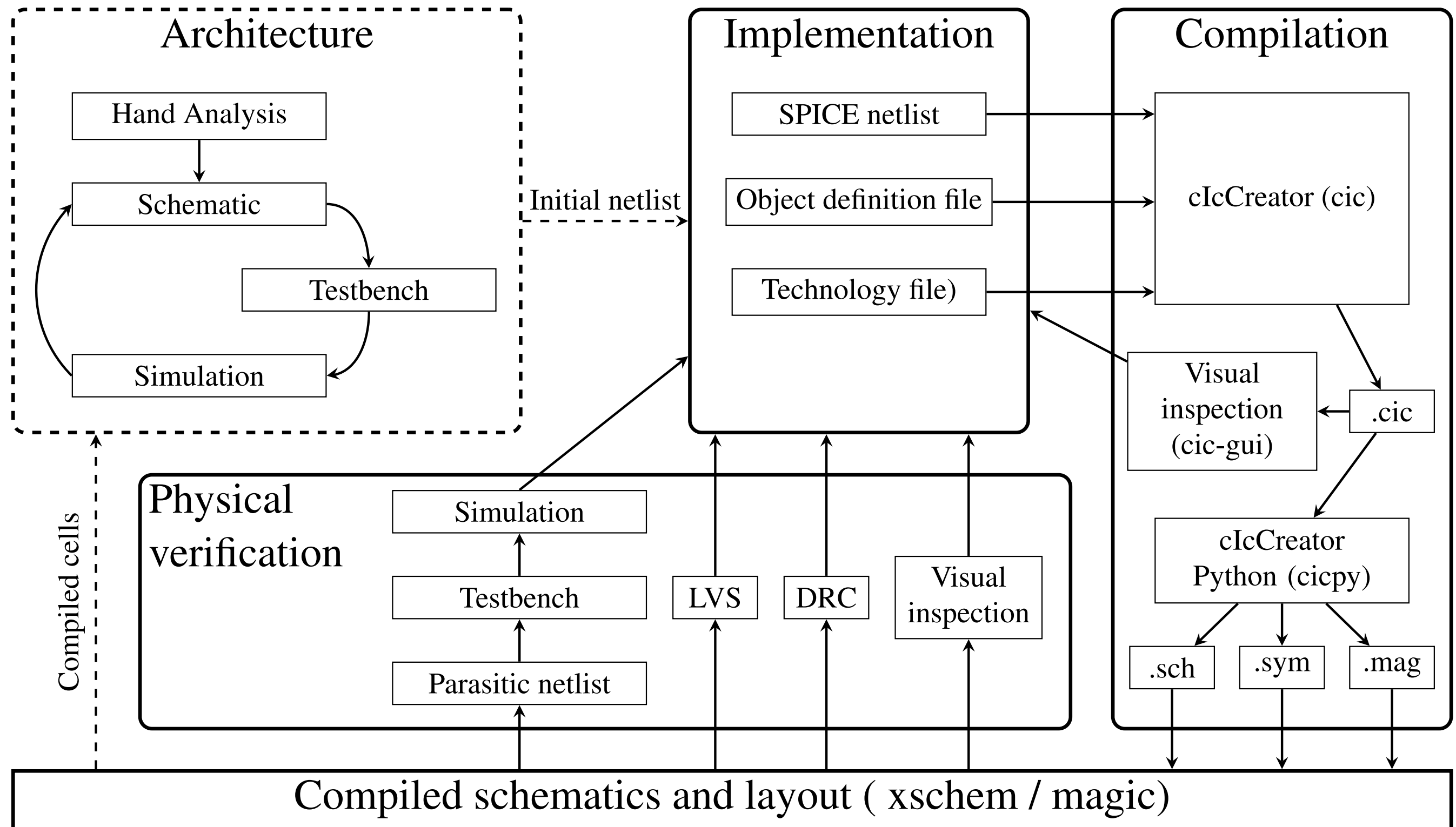
Usage is hard, requires a new type
of analog designer/programmer



ciccreator

ciccreator docs


cicpy

 


[1] A Compiled 9-bit 20-MS/s 3.5-fJ/conv.step SAR ADC in 28-nm FDSOI for Bluetooth Low Energy Receivers

[2] A 68 dB SNDR Compiled Noise-Shaping SAR ADC With On-Chip CDAC Calibration

Instance with
ADC core only.

 

ADC instance with
code correction.

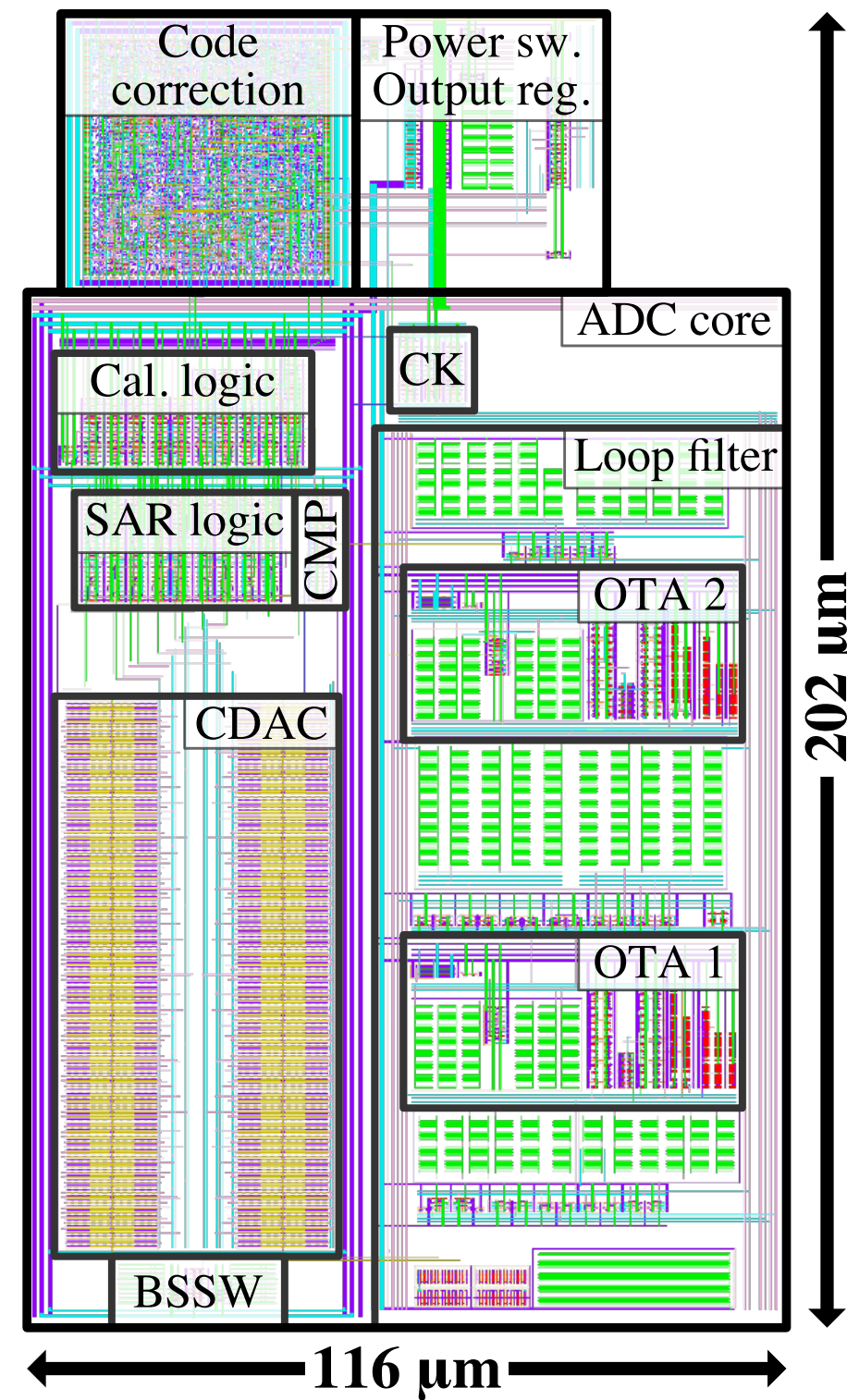

Things I want to show

- Tiny Tapeout Process
- Schematics
- Layout
- DRC/LVS
- Parasitic extraction
- Verification plan and simulations
- Delivery
- Iteration

Thanks!